

Comp3222

Tutorial 1

1. Use algebraic manipulation to prove that $(x+y)'(x+y')=x$

factoring: $(x + y)(x + y') = xy + xy'$
uniting: $xy + xy' = x$

2. Use the algebraic manipulation to prove that $xy + yz + x'z = xz + x'z$.

Dual factoring: $xy + x'z = (x+z)(x'+y)$
distributivity: $yz + x'z = (y+x')z$
distributivity: $xy + yz = (x+z)y$
 $xy + x'z + yz = (x'+y)(x+z+z) + (x+z)y$
idempotency: $x+z+z = x + z$
 $xy + x'z + yz = (x'+y)(x+z) + (x+z)y = (x'+y+y)(x+z) = (x'+y)(x+z)$
factoring: $xy + x'z + yz = xy + x'z$

3. Determine whether or not the following expression is valid:

$$x_1 * \overline{x_3} + x_2 * x_3 + \overline{x_2} * \overline{x_3} = (x_1 + \overline{x_2} + x_3)(x_1 + x_2 + \overline{x_3})(\overline{x_1} + x_2 + \overline{x_3})$$

4. Draw a timing diagram for the circuit .Show the waveforms that can be observed on all wires in the circuit.

5. Use algebraic manipulation to show that for three input variables x_1 , x_2 and x_3

$$\sum M(0, 1, 2, 3, 4, 5, 6) = x_1 x_2 x_3$$

6. Use algebraic manipulation to find the minimum product of sums expression for function

$$f = (x_1 + x_2 + x_3)(x_1 + \overline{x_2} + x_3)(\overline{x_1} + \overline{x_2} + x_3)(x_1 + x_2 + \overline{x_3})$$

7. Design the simplest circuit that has three inputs, x_1 , x_2 , and x_3 , which produces an output value of 1 whenever exactly one or two of the input variables have the value 1; otherwise the output has to be 0

8. For the timing diagram in figure, synthesize the function $f(x_1, x_2, x_3)$ in the simplest product-of-sums form.

9. For the timing diagram in figure, synthesize the function $f(x_1, x_2, x_3)$ in the simplest sum-of-products form

10. Write VHDL code to implement the function

$$f(x_1, x_2, x_3) = \sum m(0, 1, 3, 4, 5, 6)$$